

COMS3100/7100 Introduction to Communications
Sem ester 1, 20 11

Tutorial 8 Solutions

Problem 1

Consider a PLL in steady state with $\epsilon_{ss} \ll 1$ for $t < 0$. The input frequency has a step change at $t = 0$, so $\phi(t) = 2\pi f_1 t$ for $t > 0$. Solve eq [5] to find and sketch $\epsilon(t)$, assuming that $K \gg |\Delta f + f_1|$.

$\dot{\epsilon}(t) + 2\pi K \sin \epsilon(t) = 2\pi \Delta f + \dot{\phi}(t)$	[5]
$K \triangleq K_v K_a$	

Solution:

$t < 0, \quad \epsilon_{ss} = \Delta f / K$

$t > 0, \quad \dot{\phi} = 2\pi f_1$ and $\frac{\Delta f + f_1}{K} \ll 1$ so assume $|\epsilon| \ll 1$ and $\sin \epsilon \approx \epsilon$

Thus, $\dot{\epsilon} + 2\pi K \epsilon = 2\pi(\Delta f + f_1) \Rightarrow$ trial solution $\epsilon = A + B e^{st}$

Then $B s e^{st} + 2\pi K A + 2\pi K B e^{st} = 2\pi(\Delta f + f_1)$

so
$$\left. \begin{aligned} 2\pi K A &= 2\pi(\Delta f + f_1) \\ (s + 2\pi K) B e^{st} &= 0 \end{aligned} \right\} \Rightarrow \begin{cases} A = \frac{\Delta f + f_1}{K} \\ s = -2\pi K \end{cases}$$


and $\epsilon(t) = \frac{\Delta f + f_1}{K} + B e^{-2\pi K t}, \quad t > 0,$

Since $\epsilon(t)$ can make a step change at $t = 0$,

$\epsilon(0^+) = \frac{\Delta f + f_1}{K} + B = \epsilon(0^-) = \frac{\Delta f}{K} \Rightarrow B = -\frac{f_1}{K}$

Hence,

$$\epsilon(t) = \begin{cases} \frac{\Delta f}{K} & t < 0 \\ \frac{\Delta f}{K} + \frac{f_1}{K} (1 - e^{-2\pi K t}) & t > 0 \end{cases}$$

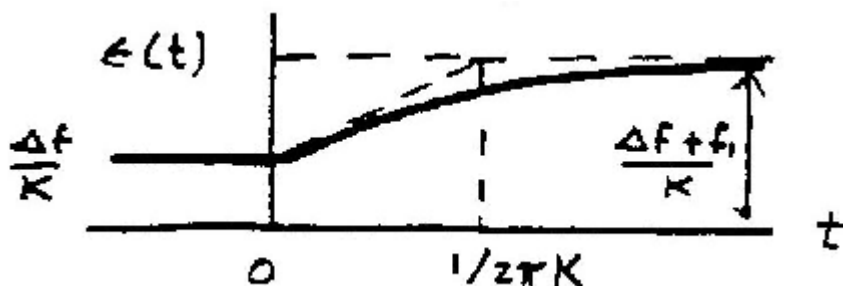

Problem 2:

Modify the FM stereo receiver in Fig. 7.2-5 to incorporate a PLL with $f_v \approx 38\text{kHz}$ for the subcarrier. Also include a dc stereo indicator.


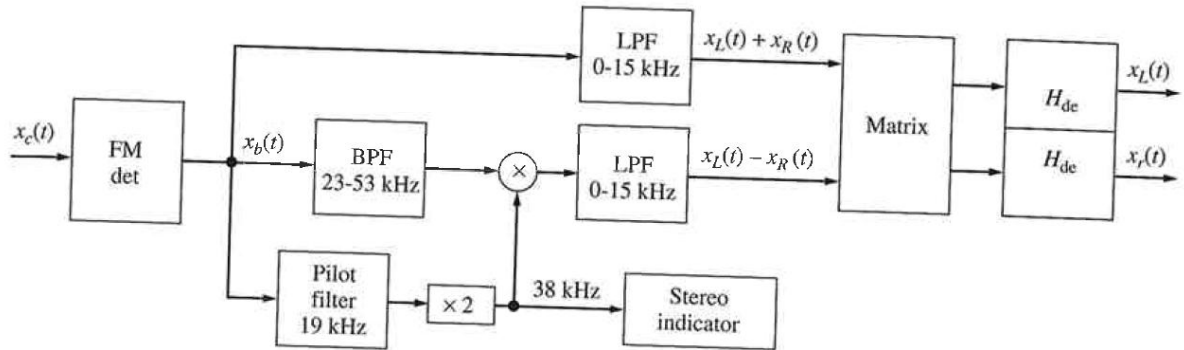


Figure 7.2-5 FM stereo multiplex receiver.

Solution:

Let subcarrier be $\cos(\omega_{sc}t + \phi_{sc})$ so pilot signal is $\cos[(\omega_{sc}t + \phi_{sc})/2]$


and output of PLL doubler will be $\cos \phi_v(t) = \cos[2(\omega_{sc}t + \phi_{sc})/2 + 2 \times 90^\circ]$

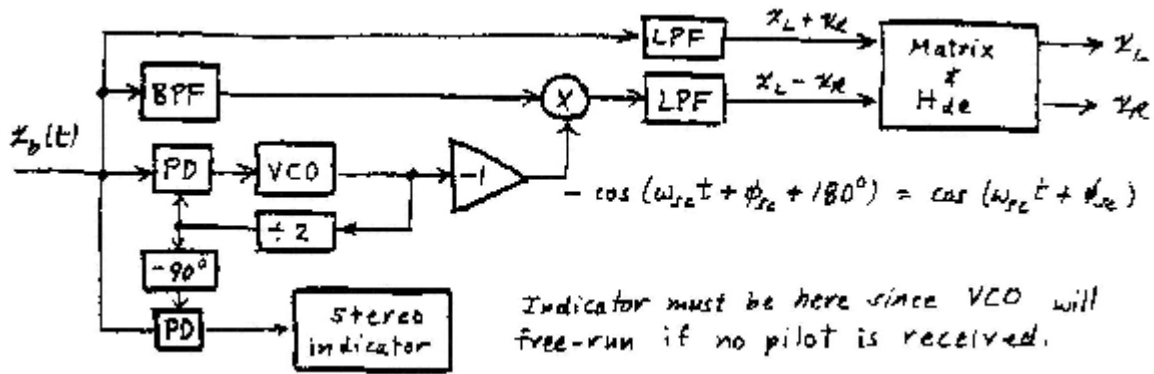

Problem 3:

Given a 100 kHz master oscillator and two adjustable divide-by-n counters with n = 1 to 10, devise a system that synthesizes any frequency from 1kHz to 99kHz in steps of 1 kHz. Specify the nominal free-running frequency of each VCO.

Solution:

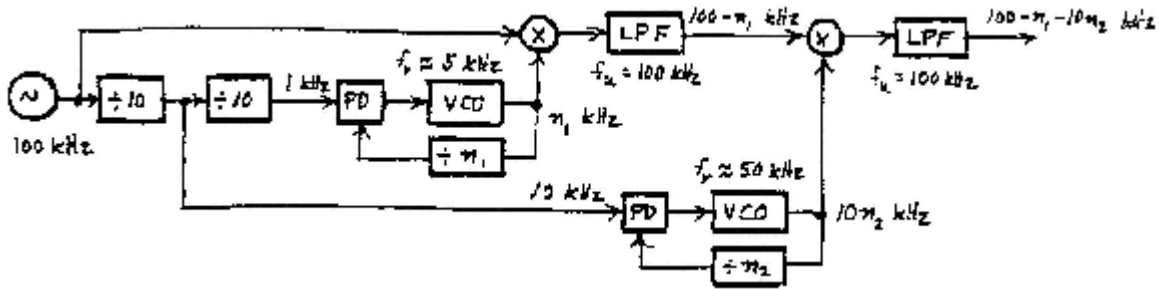

$f_v = 5\text{kHz}, 50\text{kHz}$

Problem 4:

Referring to Table 7.1-1, devise a frequency synthesizer to generate $f_{LO} = f_c + f_{IF}$ for an FM radio. Assume you have available a master oscillator at 120.0 MHz and adjustable divide-by-n counters with n = 1 to 1000.

Parameter	FM
Carrier frequency	88.1-107.9 MHz
Carrier spacing	200 kHz
Intermediate frequency	10.7 MHz
IF bandwidth	200-250 kHz
Audio bandwidth	15 kHz

Table 7.1-1

Solution:

$$f_{LO} = f_c + f_{IF} = 98.8 \text{ to } 118.6 \text{ MHz in steps of } 0.2 \text{ MHz} = 120.0 \text{ MHz} \div 600$$

$$120.0 - 98.8 = 106 \times 0.2 \text{ MHz}, \quad 120.0 - 118.6 = 7 \times 0.2 \text{ MHz}$$

